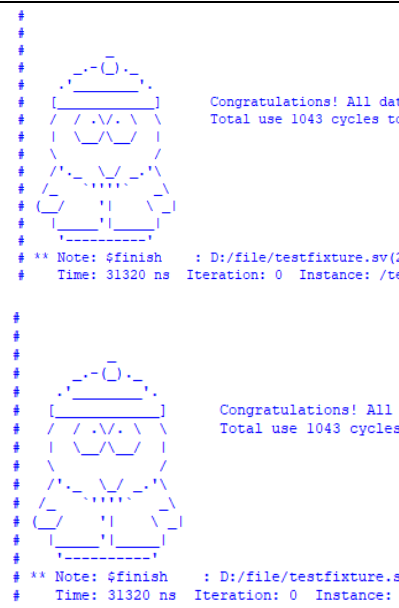
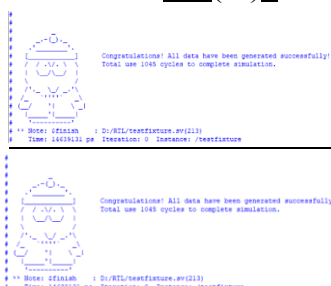

 



2025 Digital IC Design Homework 3

NAME	章元豪		
Student ID	N26132314		
Simulation Result			
Functional simulation	Pass	Pre-Layout simulation	Pass
		<p>Please specify your clock width: <u>14</u>(ns)_</p> 	
Synthesis Result			
Total logic elements	5,625/55,856(10%)		
Total memory bits	0/2,396,160(0%)		
Total registers	1266		
Embedded multiplier 9-bit elements	128/308(42%)		
Flow Summary			
 <<Filter>>			
Flow Status	Successful - Sun May 04 21:57:55 2025		
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition		
Revision Name	FFT		
Top-level Entity Name	FFT		
Family	Cyclone IV E		
Device	EP4CE55F23A7		
Timing Models	Final		
Total logic elements	5,625 / 55,856 (10 %)		
Total registers	1266		
Total pins	277 / 325 (85 %)		
Total virtual pins	0		
Total memory bits	0 / 2,396,160 (0 %)		
Embedded Multiplier 9-bit elements	128 / 308 (42 %)		
Total PLLs	0 / 4 (0 %)		

Description of your design



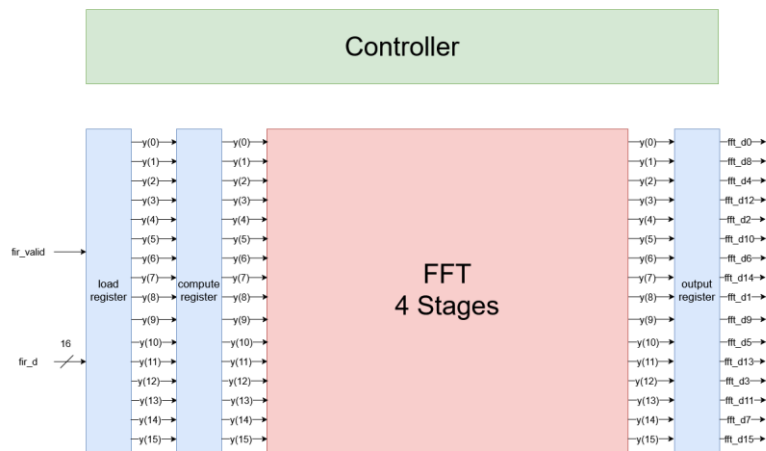我分了五個 State，初始化為 'IDLE' 階段，如果收到 TB 傳來的 fir_valid 就開始進入 'LOAD'。接完 16 筆資料就可以進入 'COMPUTE' 把資料丟給 Butterfly_Unit 來運算，算完之後在接下一組的資料期間進到 'OUTPUT'，把剛剛存在 Output 暫存器的資料輸出給 TB，然後回到 'LOAD' 繼續接資料，最後全部算完就可以進入 'DONE'。



基本上 **Butterfly_Unit** 就是按照助教的電路圖來接就行，然後接之前要睡飽或是喝咖啡，不然很容易接錯。分四個 **stage** 來計算，因為這裡涉及最多運算單元，所以會大幅度地影響到 **clock width** 。